

**IV sem (COE/IT/SE)**  
**Class Test-3 (Jan-May 2021)**  
**Digital Electronics(EC-262)**

**Time: 1 Hr**

**marks:15**

**Note: All questions are compulsory.**

1.(a) Explain the following characteristics of digital integrated circuit

- I. Figure of merit
- II. Noise Margin
- III. Fan-out

**3**

(b) Compare the performance of TTL and CMOS in terms of speed, power , noise margin and packing density.

**2**

2. Draw the circuit for CMOS NAND gate and explain its working.

**2**

3. Differentiate between Static and Dynamic RAM and draw the circuit for each type of basic RAM cell.

**3**

4. Compare the conversion time of Successive approximation type, dual slope type and flash ADC.

**2**

5. An 8 bit successive approximation ADC is to be used in an application that requires a resolution of 10 mV.

(a) What analog input range can this circuit digitize?

(b) What is the nominal full-scale input voltage?

(c) What is the binary output for an analog input of 2.00 V?

(d) What will be the conversion time for the clock signal of 1 MHz

**3**